

PLL Design and Verilog-A Behavioral Modeling Lab Report

1. PFD Verilog-A Model

```
// AMS PLL Project: Phase Frequency Detector (PFD)
`include "constants.vams"
`include "disciplines.vams"

// REF: Reference signal
// FB: Feedback signal
// UP: Up signal (FB late)
// DN: Down signal (FB early)

module PFD(REF,FB,UP,DN);
    // VDD and threshold voltage for digital signals
    parameter real VDD = 1.2;
    parameter real thresh = 0.6;
    // rise/fall/delay times of PFD output
    parameter real trise = 10p, tfall = 10p, td = 0;
    input REF,FB;
    output UP,DN;

    electrical REF,FB,UP,DN;

    // Internal UP and DN signals
    real DN_i, UP_i;
    analog begin
        // Check DN_i state when REF arrives

        @(cross(V(REF)-thresh,1))
            if(DN_i < thresh) begin
                // *** add line here ***
                UP_i = VDD;
                DN_i = 0;
            end
            else begin
                UP_i = 0;
                DN_i = 0;
            end

        // Check UP_i state when FB arrives

        @(cross(V(FB)-thresh,1))
            if(UP_i < thresh) begin
                DN_i = VDD;
            end
            else begin
```

```

        UP_i = 0;
        DN_i = 0;

    end


    V(UP) <+ transition(UP_i,td,trise,tfall);
    V(DN) <+ transition(DN_i,td,trise,tfall);

end
endmodule

```

2. PFD Testbench Results

Leading FB

 

Same Frequency ($F_{ref} = F_{fb}$)



Lagging FB

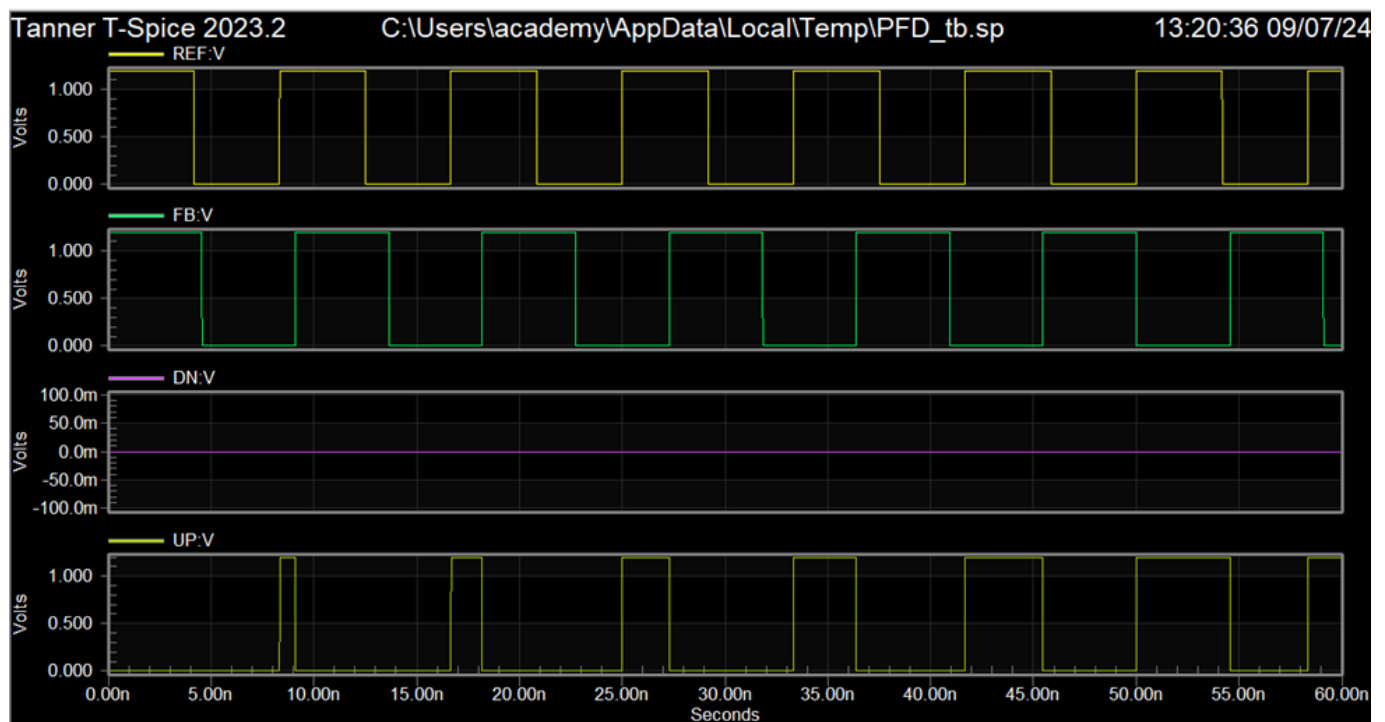


Figure: PFD operation (similar to Fig. 6.13 and Fig. 6.14 in the reference)

3. CHP Verilog-A Model

```
// AMS PLL Project: Charge Pump (CHP)
`include "constants.vams"
`include "disciplines.vams"
// UP: Up signal
// DN: Dn signal
// IOUT: CHP current output
```

```
// Since the output is current, IOOUT cannot be left unconnected (o.c.) in the
testbench

module CHP(UP,DN,IOOUT);
    input UP,DN;
    inout IOOUT;
    electrical UP,DN,IOOUT;
    // ichp: CHP current
    parameter real ichp = 10u from [0:inf);
    // Threshold voltage for digital signals
    parameter real thresh=0.6;
    // rise/fall/delay times of CHP output
    parameter real trise=10p, tfall=10p, td=0;

    // Internal variable for CHP output current

    real IOOUT_i = 0;
    analog begin
        // Generate events at UP and DN transitions
        @(cross(V(UP) - thresh, 0));
        @(cross(V(DN) - thresh, 0));
        if ((V(UP) > thresh) && (V(DN) < thresh))
            IOOUT_i = -ichp;
        else if ((V(DN) > thresh) && (V(UP) < thresh))
            IOOUT_i = ichp;
        else
            IOOUT_i = 0;
        I(IOOUT) <+ transition(IOOUT_i,td,trise,tfall);
    end
endmodule
```

4. CHP Testbench Results

 


Figure : CHP operation (similar to Fig. 6.18 in the reference)

Note: We swept for only 1n delay as it make sense that the delay won't be more than that

5. VCO Verilog-A Model

```
// AMS PLL Project: Voltage Controlled Oscillator (VCO)
`include "constants.vams"
`include "disciplines.vams"

module VCO(VCTRL,VOUT);
    parameter real VHIGH = 1.2;
    parameter real Vmin=0.2;
    parameter real Vmax=1 from (Vmin:inf);
    parameter real Fmin=0.5G from (0:inf);
    parameter real Fmax=1.5G from (Fmin:inf);
    parameter real trise=10p, tfall=10p, td=0;
    input VCTRL;
    output VOUT;
    voltage VCTRL,VOUT;
    real freq;
    real phase;
    real sine;
    real VOUT_i;

    analog begin
        // compute the freq from the input voltage
        freq = ((V(VCTRL) - Vmin)*(Fmax - Fmin) / (Vmax - Vmin)) + Fmin;
        // bound the frequency
        if (freq < Fmin) freq = Fmin;
        if (freq > Fmax) freq = Fmax;
        phase = 2 * `M_PI * idtmod(freq,0,1,-0.5);
        // generate the output
        sine = sin(phase);
        @(cross(sine,0))
        ;
        if (sine > 0)
            VOUT_i = VHIGH;
        else

            VOUT_i = 0;
        V(VOUT) <+ transition(VOUT_i,td,trise,tfall);
        // bound the time step

        $bound_step(1 / (freq * 100));
    end
endmodule
```

6. VCO Testbench Results

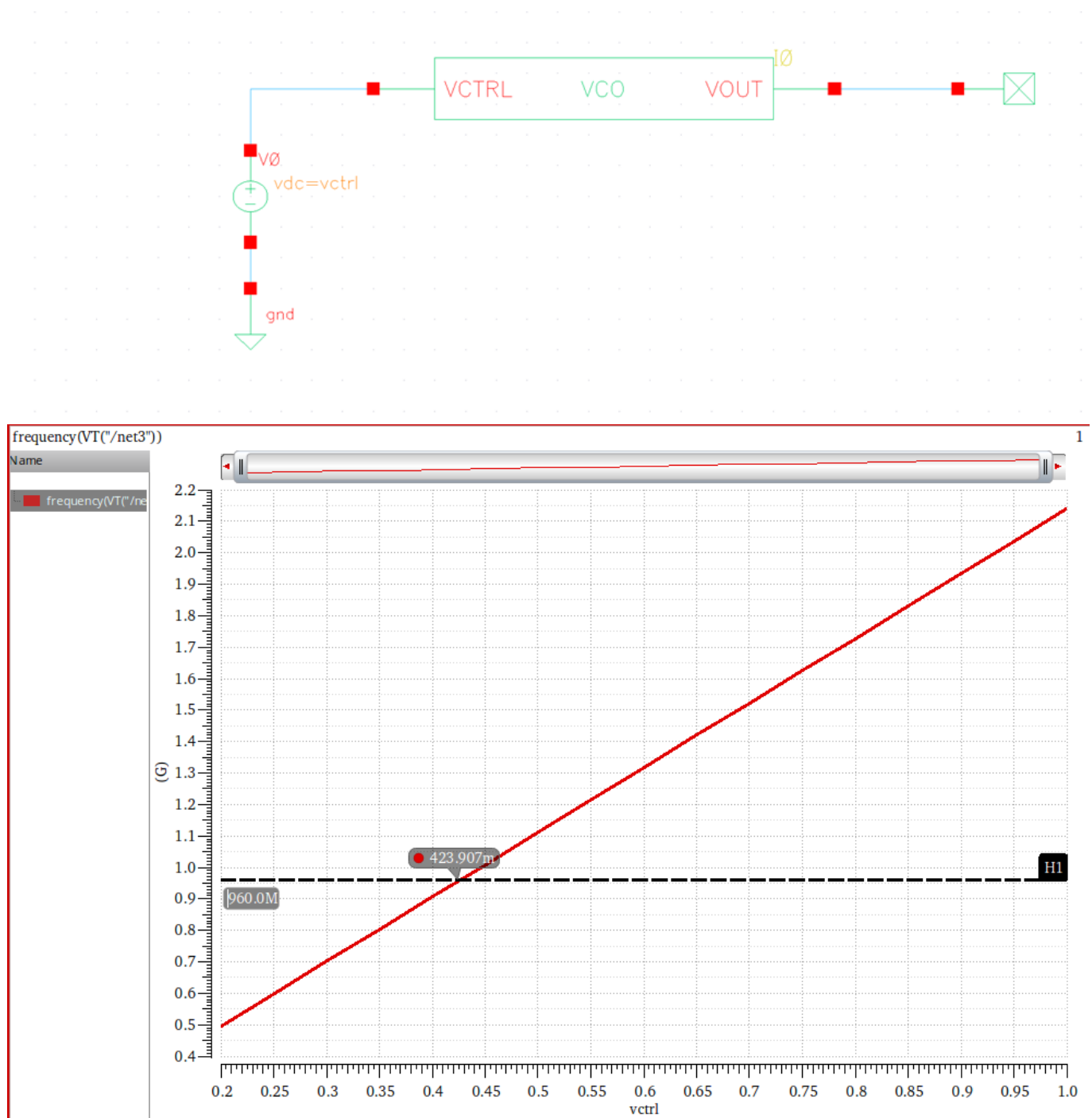


Figure : VCO operation (similar to Fig. 6.11 in the reference)

7. Divider Verilog-A Model

```
// AMS PLL Project: Frequency Divider
`include "constants.vams"
`include "disciplines.vams"

module Divider(VIN,VOUT);

    output VOUT; voltage VOUT; // output
    input VIN; voltage VIN; // input (edge triggered)
    parameter real vh=1.2; // output voltage in high state
    parameter real vl=0; // output voltage in low state
```

```
parameter real vth=0.6; // threshold voltage at input
parameter integer ratio=8 from [2:inf); // divider ratio
parameter real tt=10p from (0:inf); // transition time of output signal
parameter real td=0 from [0:inf); // average delay from input to output

// *** add line here ***
real count=0;
real out_value=0;

analog begin

    @(cross(V(VIN) - vth, 1)) begin
        if (count==floor(ratio/2))
            out_value = vh;

        if (count == floor(ratio))begin
            out_value = vl;
            count = 0;
        end

        count = (count + 1);
    end

    V(VOUT) <+ transition(out_value, td, tt);

end
endmodule
```

8. Divider Testbench Results (Verilog-A)

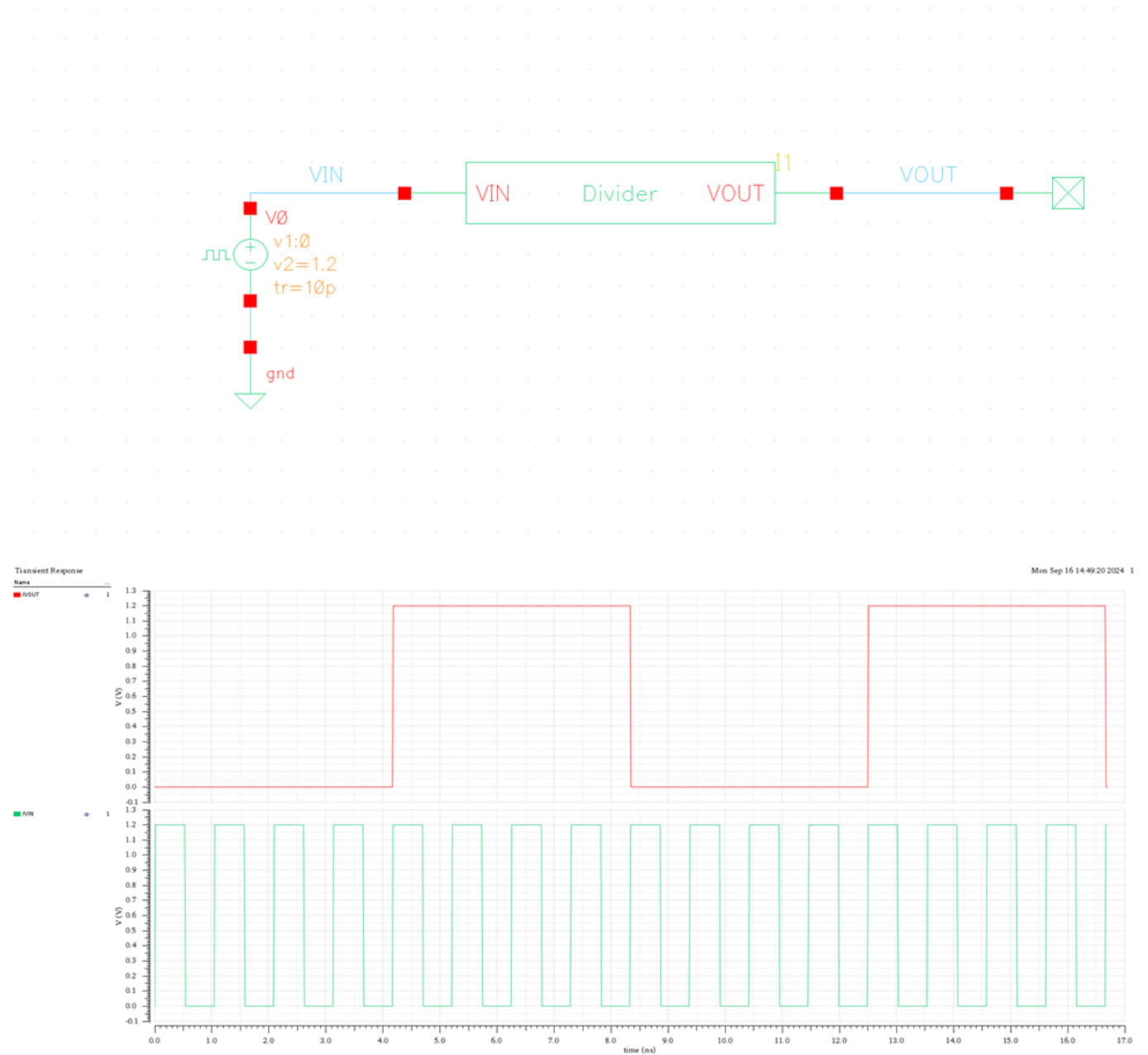


Figure : Divider operation using Verilog-A model (similar to Fig. 6.20 in the reference)

9. Transistor-Level Divider Design

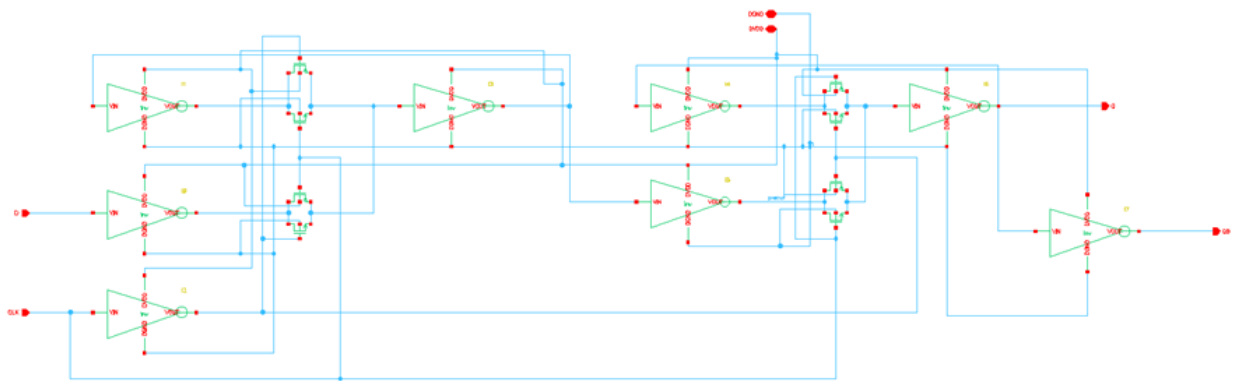
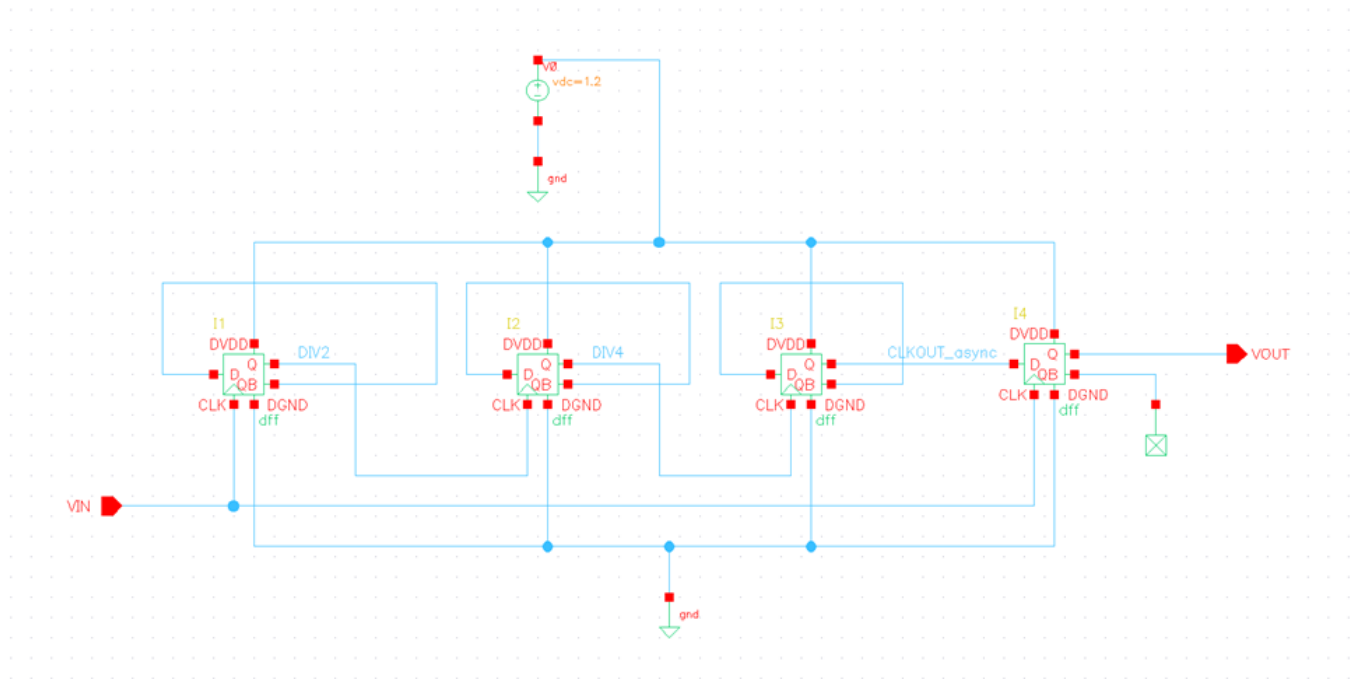


Figure : Transistor-level schematic of the DFF used in the divider design

10. Transistor-Level Divider Testbench Results

 


Figure : Divider operation using transistor-level design (similar to Fig. 6.20 in the reference)

11. Complete PLL Simulation (Verilog-A Models) (VCTRL)

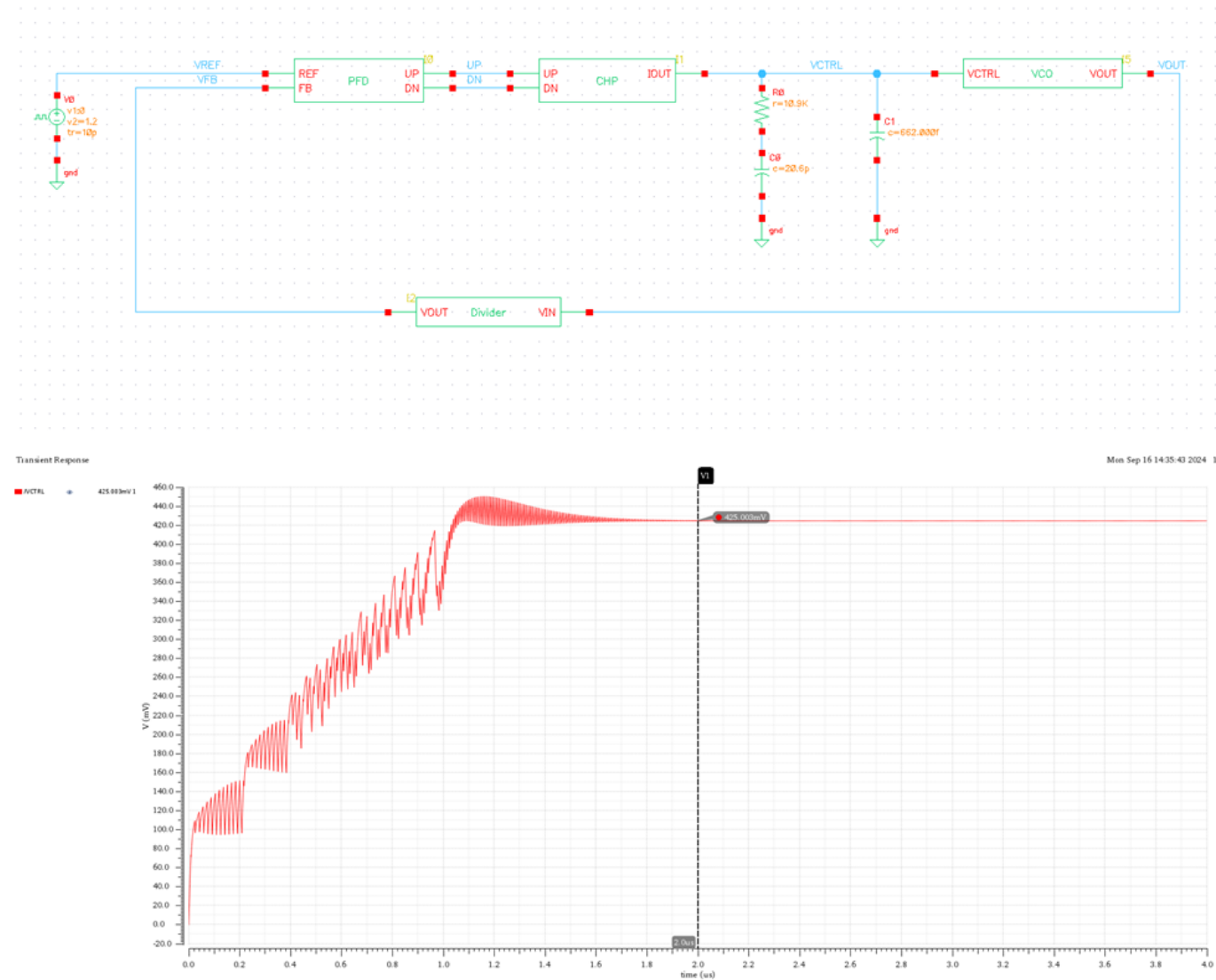


Figure : VCO control voltage (similar to Fig. 6.7 in the reference)

Vctrl @ lock = 0.425mV

12. Analytical Calculation of Control Voltage at Lock

The equation for (K_{vco}) is:

$$[K_{vco} = \frac{f_{\text{out}} - f_{\text{min}}}{V_{\text{ctrl}} - V_{\text{min}}}]$$

The equation for (V_{ctrl}) is:

$$[V_{\text{ctrl}} = \frac{f_{\text{out}} - f_{\text{min}}}{K_{vco}} + V_{\text{min}}]$$

Given that:

$$[V_{\text{ctrl}} = 0.4244]$$

13. Comparison of Simulated vs. Calculated Control Voltage

	Simulated Value	Calculated Value
VCTRL	0.4244	0.425

Comment: The two results match each other.

14. Complete PLL Operation (Verilog-A Models) (ALL SIGNALS)

 


Figure : PLL operation (similar to Fig. 6.8 in the reference)

Period of Ref: 8.33n Period of VOUT: 1.0412n

15. Simulation Log (Verilog-A Models)

```
SUBCKTS. Writing subcircuits to rawfile.

Aggregate audit (4:00:15 PM, Mon Sep 16, 2024):
Time used: CPU = 7.88 s, elapsed = 7.89 s, util. = 99.9%.
Time spent in licensing: elapsed = 67.6 ms.
Peak memory used = 158 Mbytes.
Simulation started at: 4:00:07 PM, Mon Sep 16, 2024, ended at: 4:00:15 PM, Mon Sep 16, 2024, with elapsed time (wall clock): 7.89 s.
spectre completes with 0 errors, 2 warnings, and 1 notice.
```

16. Updated Hierarchy with Schematic Divider

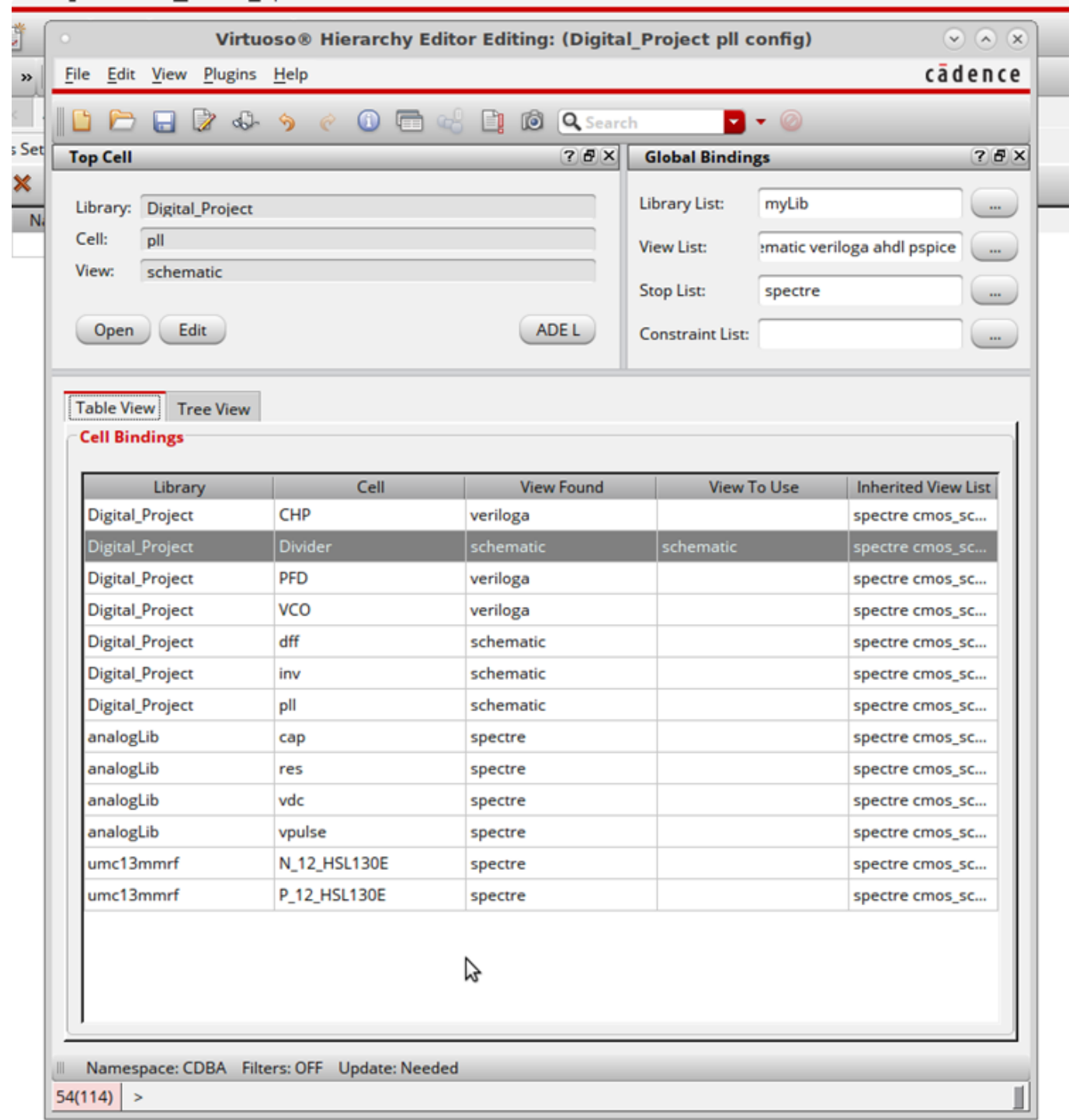


Figure : Configuration in hierarchy editor with schematic view of divider

17. PLL Simulation with Transistor Level (Control Voltage)


 


Figure : VCO control voltage with schematic divider (similar to Fig. 6.23 in the reference)

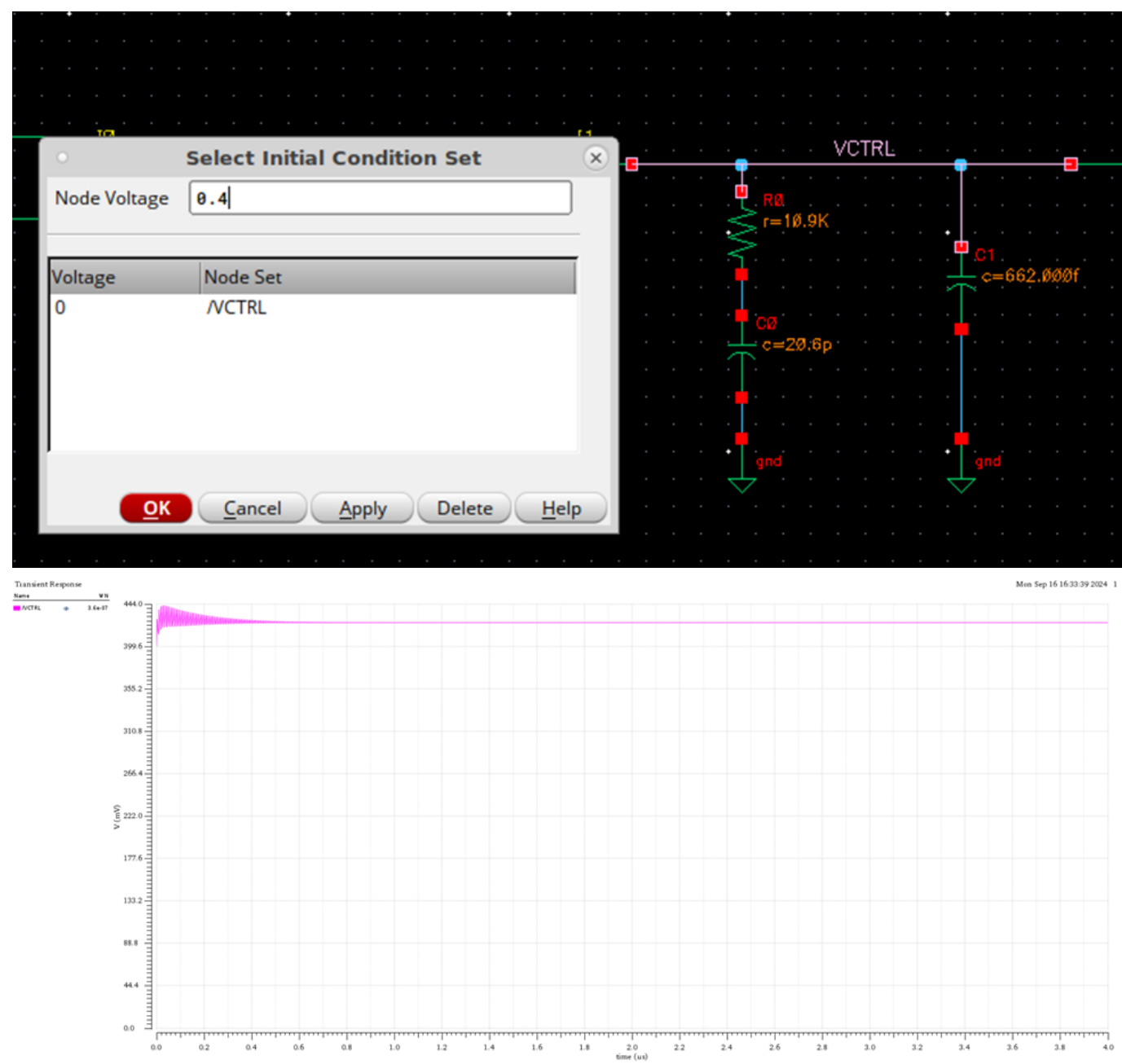Note: Different to the one in pll document due to initial condition, we could achieve the same if we put IC on capacitor.



18. PLL Operation with Transistor Level Divider (ALL SIGNALS)

 


Figure 11: PLL operation with schematic divider (similar to Fig. 6.24 in the reference)

Period of Ref: 8.33n Period of VOUT: 1.04n

19. Simulation Log (with Schematic Divider)

```
Aggregate audit (3:51:48 PM, Mon Sep 16, 2024):
Time used: CPU = 218 s (3m 37.6s), elapsed = 218 s (3m 37.7s), util. = 100%.
Time spent in licensing: elapsed = 68.7 ms.
Peak memory used = 191 Mbytes.
Simulation started at: 3:48:10 PM, Mon Sep 16, 2024, ended at: 3:51:48 PM, Mon Sep 16, 2024, with elapsed time (wall clock): 218 s (3m 37.7s).
spectre completes with 0 errors, 11 warnings, and 10 notices.
```

20. Simulation Time Comparison

	Behavioral	Transistor Level
Simulation Time	7.9 Seconds	3 Minutes and 38 Seconds

Comment: There is a huge difference between the Transistor level simulation and Behavior level simulation results, we can see the advantage of simulating complex systems using top-down

methodology with behavioral models to decrease simulation time and verify that the system will work before implementing and wasting time on something that will not work and not achievable.